

Network Theorems in Terms of Graph Theory

KCL:

$$A_a I_b = 0$$

$$A I_b = 0$$

$$Q I_b = 0$$

KVL:

$$B V_b = 0$$

Relation between
branch voltage
and node voltage


$$V_b = A^T V_n$$

\downarrow branch voltage \downarrow node voltage

Relation between
branch current and
loop current:

$$I_b = B^T I_L$$

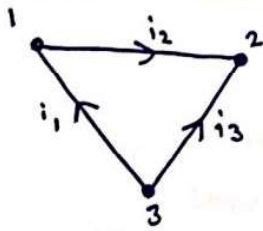\downarrow branch current \downarrow loop current



$$-i_1 + i_2 = 0 \quad \text{--- (1)}$$

$$-i_2 - i_3 = 0 \quad \text{--- (2)}$$

$$i_1 + i_3 = 0 \quad \text{--- (3)}$$


Complete Incidence
matrix

$$A_a = \begin{matrix} & \begin{matrix} (1) & (2) & (3) \end{matrix} \\ \begin{matrix} 1 \\ 2 \\ 3 \end{matrix} & \begin{bmatrix} -1 & 1 & 0 \\ 0 & -1 & -1 \\ 0 & 0 & 1 \end{bmatrix} \end{matrix}$$

$$A I_b = \begin{bmatrix} -1 & 1 & 0 \\ 0 & -1 & -1 \\ 0 & 0 & 1 \end{bmatrix} \begin{bmatrix} i_1 \\ i_2 \\ i_3 \end{bmatrix} = 0 \quad \left[\text{According to KCL of graph theory} \right]$$

$$= \begin{bmatrix} -i_1 + i_2 \\ -i_2 - i_3 \\ i_1 + i_3 \end{bmatrix}$$

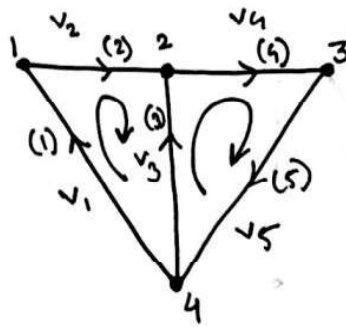
$$= 0 \quad \left[\text{Proved} \right]$$



$$v_1 + v_2 - v_3 = 0 \quad \text{--- (1)}$$

$$v_3 + v_4 + v_5 = 0 \quad \text{--- (2)}$$

Consider the Tree —

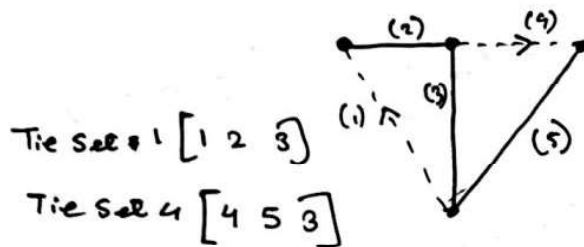


$$B = \begin{matrix} & (1) & (2) & (3) & (4) & (5) \\ \begin{matrix} TS1 \\ TS4 \end{matrix} & \begin{bmatrix} 1 & 1 & -1 & 0 & 0 \\ 0 & 0 & 1 & 1 & 1 \end{bmatrix} \end{matrix}$$

According to KVL of graph theory $\rightarrow BV_b = 0 = \begin{bmatrix} 1 & 1 & -1 & 0 & 0 \\ 0 & 0 & 1 & 1 & 1 \end{bmatrix} \begin{bmatrix} v_1 \\ v_2 \\ v_3 \\ v_4 \\ v_5 \end{bmatrix}$

$$\therefore \begin{bmatrix} v_1 + v_2 - v_3 \\ v_3 + v_4 + v_5 \end{bmatrix} = 0 \quad [\text{Proved}]$$

Mesh Law

Kth branch

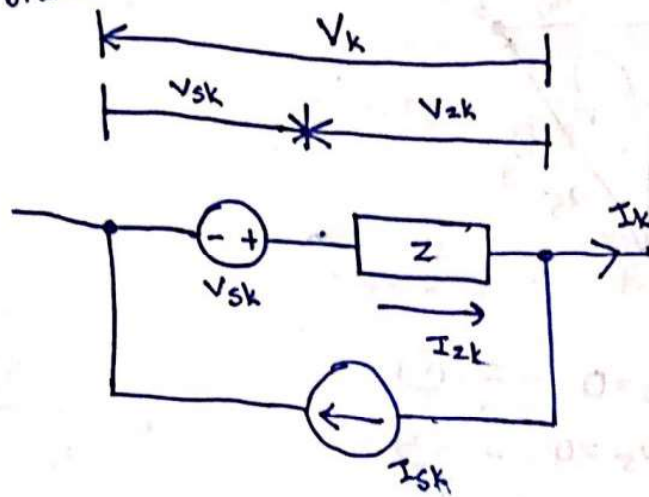

$$V_K = V_{ZK} - V_{SK}$$

$$\text{or, } V_{SK} + V_K = V_{ZK} = (Z_K)(I_{ZK}) = Z_K(I_K + I_{SK})$$

for branch 1,

$$V_{S1} + V_1 = (Z_1)(I_1 + I_{S1})$$

for branch 2,

$$V_{S2} + V_2 = (Z_2)(I_2 + I_{S2})$$

...

for branch b,

$$V_{Sb} + V_b = (Z_b)(I_b + I_{Sb})$$

$$\begin{matrix} \text{Source voltage} \\ \text{matrix} \end{matrix} \begin{bmatrix} V_{S1} \\ V_{S2} \\ V_{S3} \\ \vdots \\ V_{Sb} \end{bmatrix} + \begin{matrix} \text{branch matrix} \\ \text{voltage} \end{matrix} \begin{bmatrix} V_1 \\ V_2 \\ V_3 \\ \vdots \\ V_b \end{bmatrix} = \begin{matrix} \text{Impedance} \\ \text{matrix} \end{matrix} \begin{bmatrix} Z_1 & 0 & 0 & \dots \\ 0 & Z_2 & & \\ & & Z_3 & \\ & & & \ddots \\ 0 & 0 & & & Z_b \end{bmatrix} \left(\begin{bmatrix} I_1 \\ I_2 \\ I_3 \\ \vdots \\ I_b \end{bmatrix} + \begin{bmatrix} I_{S1} \\ I_{S2} \\ I_{S3} \\ \vdots \\ I_{Sb} \end{bmatrix} \right)$$

KVL Equation for bth branch,


$$V_{sb} + V_b = (Z_b)(I_b + I_{sb}) \dots \text{--- ①}$$

$$B V_{sb} + B \downarrow_0 V_b = B Z_b (I_b + I_{sb})$$


$$B V_{sb} = B Z_b I_b + B Z_b I_{sb}$$

$$\text{or, } B Z_b I_b = B (V_{sb} - Z_b I_{sb})$$

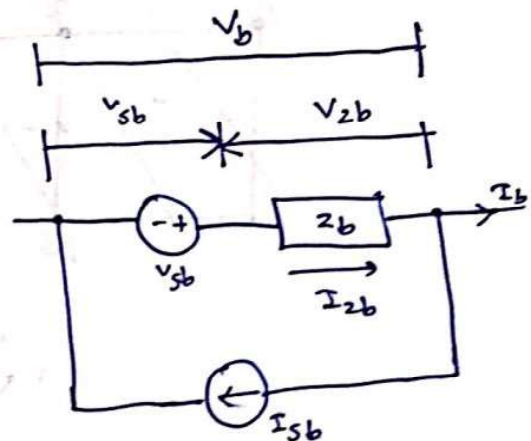
$$\text{or, } \boxed{B Z_b B^T I_L = B (V_{sb} - Z_b I_{sb})}$$



Mesh Law
for Graph Theory


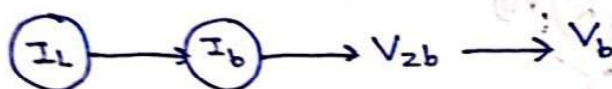


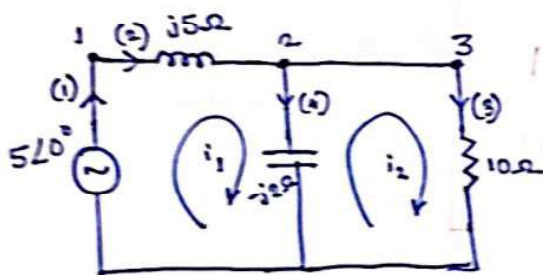Problem: Derive the Mesh Equation in terms of Graph Theory for the circuit shown below.




$$V_{sb} = \begin{bmatrix} 5 \\ 0 \\ 0 \\ 0 \end{bmatrix} \quad I_{sb} = 0$$
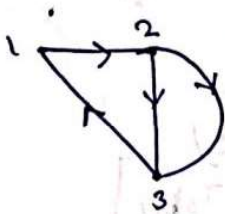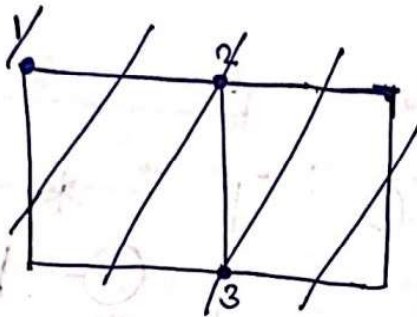
$$Z_b = \begin{bmatrix} & (1) & (2) & (3) & (4) \\ & 0 & 0 & 0 & 0 \\ & 0 & j5 & 0 & 0 \\ & 0 & 0 & 10 & 0 \\ & 0 & 0 & 0 & -j2 \end{bmatrix}$$



Take tree as —

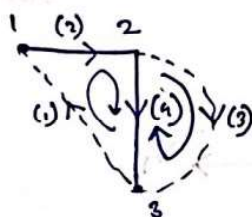

Tie set 1 [1 2 3]

Tie set 3 [3 2]

$$B = \begin{matrix} & \begin{matrix} (1) & (2) & (3) & (4) \end{matrix} \\ \begin{matrix} T_{S1} \\ T_{S3} \end{matrix} & \begin{bmatrix} 1 & 1 & 0 & 1 \\ 0 & 0 & 1 & -1 \end{bmatrix} \end{matrix}$$

$$\therefore \text{RHS} = BV_{sb} = \begin{bmatrix} 1 & 1 & 0 & 1 \\ 0 & 0 & 1 & -1 \end{bmatrix}_{2 \times 4} \begin{bmatrix} 5 \\ 0 \\ 0 \\ 0 \end{bmatrix}_{4 \times 1} = \begin{bmatrix} 5 \\ 0 \end{bmatrix}_{2 \times 1}$$

$$\text{LHS} = \begin{bmatrix} 1 & 1 & 0 & 1 \\ 0 & 0 & 1 & -1 \end{bmatrix}_{2 \times 4} \begin{bmatrix} 0 & 0 & 0 & 0 \\ 0 & j5 & 0 & 0 \\ 0 & 0 & 10 & 0 \\ 0 & 0 & 0 & -j2 \end{bmatrix}_{4 \times 4} \begin{bmatrix} 1 & 0 \\ 1 & 0 \\ 0 & 1 \\ 1 & -1 \end{bmatrix}_{4 \times 2} \begin{bmatrix} i_1 \\ i_2 \end{bmatrix}_{2 \times 1}$$



$$= \begin{bmatrix} j3 & j2 \\ j2 & 10-j2 \end{bmatrix} \begin{bmatrix} i_1 \\ i_2 \end{bmatrix}$$

∴ Mesh Equation:

$$\begin{bmatrix} j3 & j2 \\ j2 & 10-j2 \end{bmatrix} \begin{bmatrix} i_1 \\ i_2 \end{bmatrix} = \begin{bmatrix} 5 \\ 0 \end{bmatrix}$$

∴ LHS = RHS [Proved]

Two Port Networks

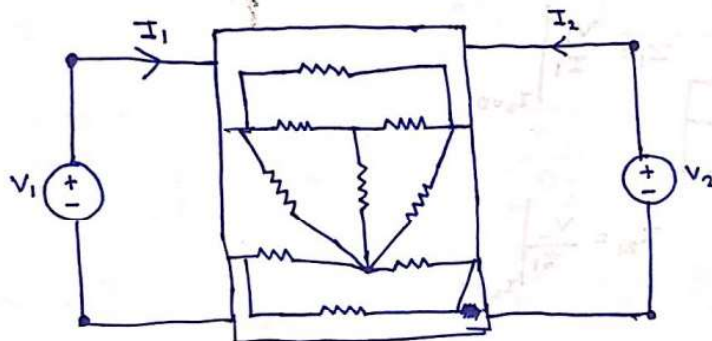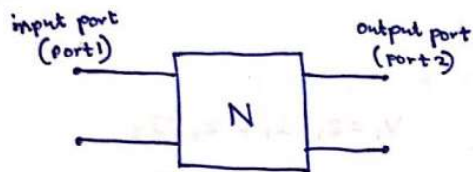

<u>Dependent Variable</u>	<u>Independent Variable</u>
V_1, V_2	I_1, I_2
I_1, I_2	V_1, V_2
V_1, I_1	V_2, I_2
V_1, I_2	I_1, V_2
V_2, I_2	V_1, I_1
I_1, V_2	V_1, I_2

Z-Parameter

$$V_1 = f(I_1, I_2)$$

$$V_2 = f(I_1, I_2)$$

Definition
Equation
of
z-parameter

$$V_1 = Z_{11} I_1 + Z_{12} I_2 \quad \text{--- (1)}$$

$$V_2 = Z_{21} I_1 + Z_{22} I_2 \quad \text{--- (2)}$$


$$[Z] = \begin{bmatrix} Z_{11} & Z_{12} \\ Z_{21} & Z_{22} \end{bmatrix}$$

input dragging point impedance
backwards/reverse transfer impedance

forward transfer impedance

output dragging point impedance

• Finding the z-parameters —

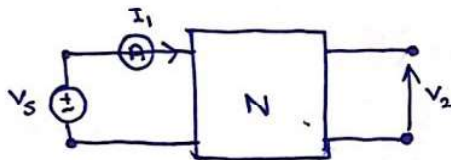

$$V_1 = Z_{11} I_1 + Z_{12} I_2$$


$$V_2 = Z_{21} I_1 + Z_{22} I_2$$

$$V_1 = V_s$$

V_1	V_2	I_1	I_2
V	V	V	0

$$Z_{11} = \left. \frac{V_1}{I_1} \right|_{I_2=0}$$

$$Z_{21} = \left. \frac{V_2}{I_1} \right|_{I_2=0}$$

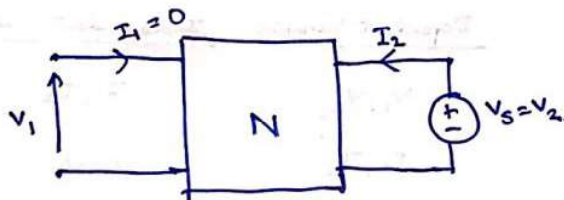


• open circuit impedance
parameter → symbol: Z

V_1	V_2	I_1	I_2
V	V	0	V

$$Z_{12} = \left. \frac{V_1}{I_2} \right|_{I_1=0}$$

$$Z_{22} = \left. \frac{V_2}{I_2} \right|_{I_1=0}$$

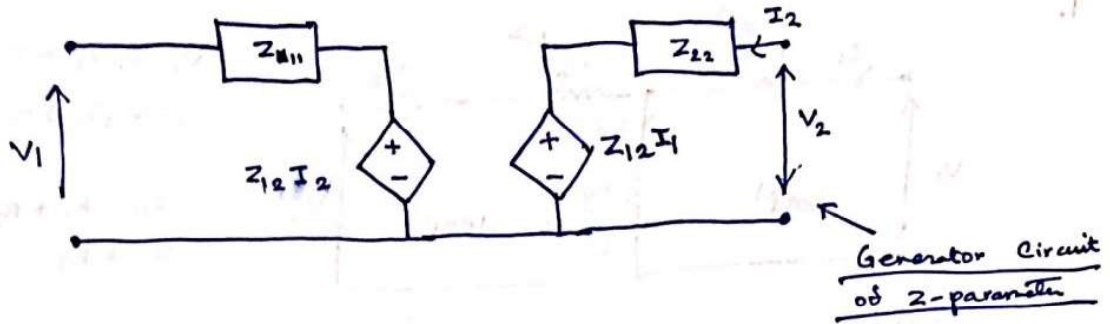

Y-Parameter

$$I_1 = f(V_1, V_2)$$

$$I_2 = f(V_1, V_2)$$

~~Same as~~



$$\begin{cases} I_1 = Y_{11} V_1 + Y_{12} V_2 \dots \dots \textcircled{1} \\ I_2 = Y_{21} V_1 + Y_{22} V_2 \dots \dots \textcircled{2} \end{cases}$$

Same as Z (is admittance in place of impedance)

$Y_{11}, Y_{12}, Y_{21}, Y_{22} \rightarrow$ Admittance

$Y \rightarrow$ Short Circuit Admittance parameter

$\rightarrow Y$ parameter

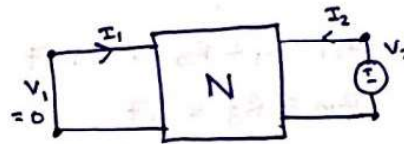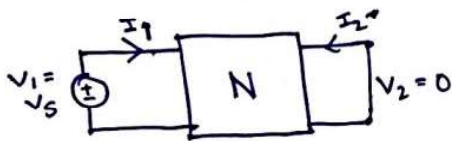

V_1	V_2	I_1	I_2
	0		

V_1	V_2	I_1	I_2
0			

$$Y_{11} = \frac{I_1}{V_1} \bigg|_{V_2=0}$$


$$Y_{21} = \frac{I_2}{V_1} \bigg|_{V_2=0}$$

$$Y_{12} = \frac{I_1}{V_2} \bigg|_{V_1=0}$$

$$Y_{22} = \frac{I_2}{V_2} \bigg|_{V_1=0}$$

Problem:

1.

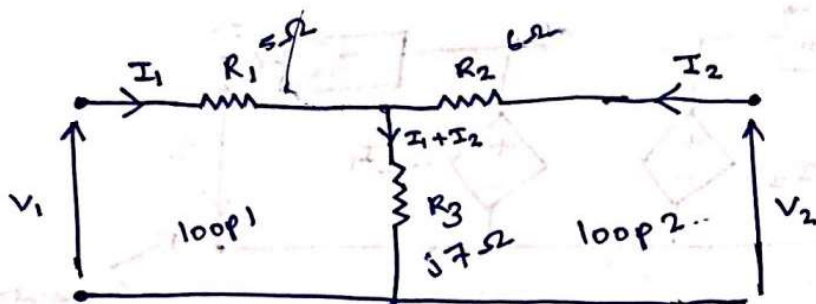

$$V_1 = Z_{11} I_1 + Z_{12} I_2 \dots$$

$$V_2 = Z_{21} I_1 + Z_{22} I_2 \dots$$

$$Z_{11} = R_1 + R_3$$

$$Z_{12} = R_3$$

for loop 1

$$V_1 = I_1 R_1 + R_3 (I_1 + I_2)$$

$$\text{or, } V_1 = (R_1 + R_3) I_1 + R_3 I_2 \dots \dots \textcircled{1}$$

$$Z_{11} = 5 + j7$$

$$Z_{12} = j7$$

for loop 2

$$V_2 = I_2 R_2 + (I_1 + I_2) R_3$$


$$\text{or, } V_2 = R_3 I_1 + (R_2 + R_3) I_2 \dots \dots \textcircled{2}$$

$$\therefore Z_{11} = R_1 + R_3 = 5 + j7$$

$$Z_{12} = R_3 = j7$$

$$Z_{21} = R_3 = j7$$
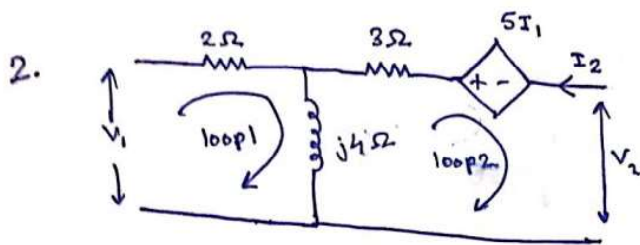
$$Z_{22} = R_2 + R_3 = 6 + j7 \quad (\text{Ans})$$



Defn of Z parameter :

$$V_1 = Z_{11} I_1 + Z_{12} I_2 \dots \dots \textcircled{1}$$

$$V_2 = Z_{21} I_1 + Z_{22} I_2 \dots \dots \textcircled{2}$$

For loop 1 by applying KVL,

$$V_1 = 2I_1 + j4(I_1 + I_2)$$

$$V_1 = (2 + j4)I_1 + j4I_2 \dots \dots \textcircled{i}$$

$$Z_{11} = (2 + j4)\Omega$$

$$Z_{12} = j4\Omega$$

$$V_2 \neq 5I_1 = 3I_2 + j4(I_1 + I_2)$$


$$V_2 = (-5 + j4)I_1 + (3 + j4)I_2 \dots \dots \textcircled{ii}$$

$$Z_{21} = (-5 + j4)\Omega$$

$$Z_{22} = (3 + j4)\Omega$$

$$[Z] = \begin{bmatrix} 2 + j4 & j4 \\ -5 + j4 & 3 + j4 \end{bmatrix} \text{ (Ans)}$$

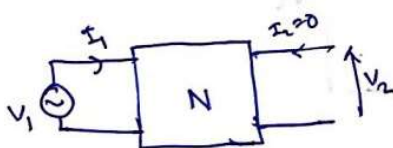ABCD Parameter or Transmission Parameter or T-Parameter



Defn of T-parameter:

$$V_1 = AV_2 + B(-I_2) \dots \dots \textcircled{1}$$

$$I_1 = CV_2 + D(-I_2) \dots \dots \textcircled{2}$$

From equation ①,

$$V_1 = AV_2$$

$$\therefore A = \left. \frac{V_1}{V_2} \right|_{I_2=0}$$


Unit of A \rightarrow Unitless

From equation ②,

$$I_1 = CV_2$$

$$\Rightarrow C = \left. \frac{I_1}{V_2} \right|_{I_2=0}$$

Unit of C $\rightarrow \Omega$

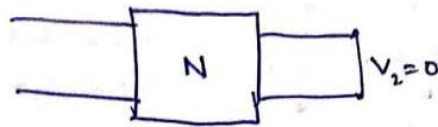

from equation ①,

$$V_1 = B(-I_2)$$


$$\Rightarrow B = \left. \frac{V_1}{-I_2} \right|_{V_2=0} \quad \text{Unit of } B \rightarrow \Omega$$

from equation ②,

$$I_1 = D(-I_2)$$


$$\therefore D = \left. \frac{I_1}{-I_2} \right|_{V_2=0} \quad \text{Unit of } D \rightarrow \text{Unitless}$$

Find out ABCD Parameter —

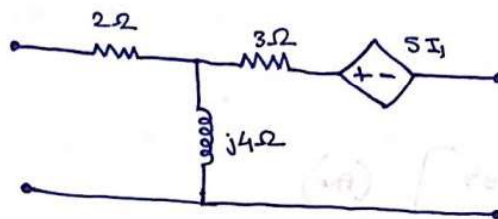

$$[T] = \begin{bmatrix} A & B \\ C & D \end{bmatrix} = \begin{bmatrix} 2+j4 \\ -5+j4 \end{bmatrix}$$

Step 1:

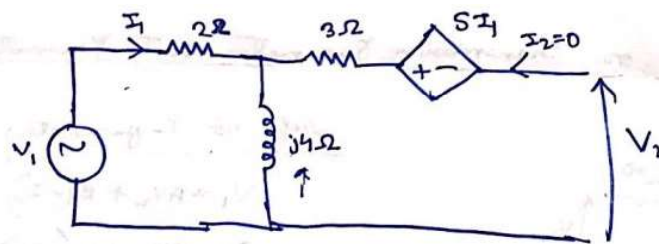

$$V_1 - 2I_1 - (I_1 - 5I_1)j4 = 0$$

$$V_1 = (2+j4)I_1 + j4I_2 \quad \text{--- ①}$$

$$V_2 = (-5+j4)I_1 + (3+j4)I_2 = 0$$

$$\underline{I_2 = 0}$$

$$V_1 = (2+j4)I_1 \quad \cancel{\neq} \quad \frac{I_1}{V_1} = \cancel{\neq} \quad \frac{1}{2+j4}$$

$$V_2 = (-5+j4)I_1 \Rightarrow \frac{I_1}{V_2} = C = \frac{1}{-5+j4} \quad (\text{Ans})$$

$$\therefore A = \frac{V_1}{V_2} = \frac{2+j4}{-5+j4} \text{ (Ans)}$$

$$\therefore \underline{V_2 = 0}$$

$$0 = (-5+j4)I_1 + (3+j4)I_2$$

$$\Rightarrow \frac{I_1}{I_2} = \frac{3+j4}{5-j4}$$

$$\Rightarrow (5-j4)I_1 = (3+j4)I_2$$

$$\Rightarrow \frac{I_1}{I_2} = \frac{3+j4}{5-j4} \Rightarrow \frac{I_1}{-I_2} = \frac{3+j4}{-5+j4}$$

$$\therefore \text{In (i),}$$

$$V_1 = (2+j4) \frac{(3+j4)}{(5-j4)} I_2 + j4 I_2$$

$$\Rightarrow \frac{V_1}{I_2} = \frac{(2+j4)(3+j4)}{(5-j4)} + j4$$

$$\Rightarrow \frac{V_1}{I_2} = \frac{6+2j4+3j4-16}{5-j4} + j4$$

$$= \frac{-10+j20}{5-j4} + j4$$

$$= \frac{j20-10+20j+16}{5-j4}$$

$$= \frac{j40+16}{5-j4}$$

h-Parameter or hybrid parameter


$$V_1 = f(I_1, V_2)$$

$$I_2 = f(I_1, V_2)$$


definition:

$$V_1 = h_{11} I_1 + h_{12} V_2 \dots \dots \textcircled{1}$$
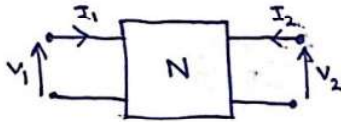
$$I_2 = h_{21} I_1 + h_{22} V_2 \dots \dots \textcircled{2}$$



1) Take $V_2 = 0$

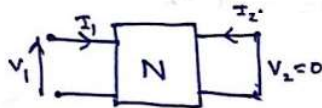


$$\textcircled{1} \Rightarrow V_1 = h_{11} I_1$$

$$\Rightarrow h_{11} = \left. \frac{V_1}{I_1} \right|_{V_2=0} \quad \text{Unit: } \Omega$$

$$\textcircled{2} \Rightarrow I_2 = h_{21} I_1$$

$$\therefore h_{21} = \left. \frac{I_2}{I_1} \right|_{V_2=0} \quad \text{Unitless}$$

2) Take $I_1 = 0$

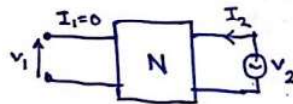


$$\textcircled{1} \Rightarrow V_1 = h_{12} V_2$$

$$\therefore h_{12} = \left. \frac{V_1}{V_2} \right|_{I_1=0} \quad \text{Unitless}$$

$$\textcircled{2} \Rightarrow I_2 = h_{22} V_2$$


$$\therefore h_{22} = \left. \frac{I_2}{V_2} \right|_{I_1=0} \quad \text{Unit: } \Omega$$

Find out h-parameter

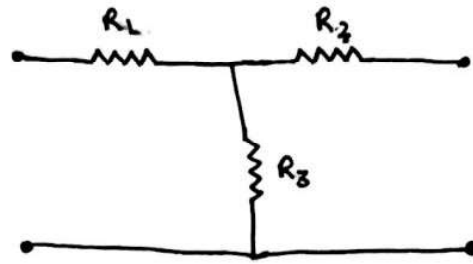


$$\therefore V_1 = I_1 R_1 + (I_1 + I_2) R_3 \dots \textcircled{3}$$
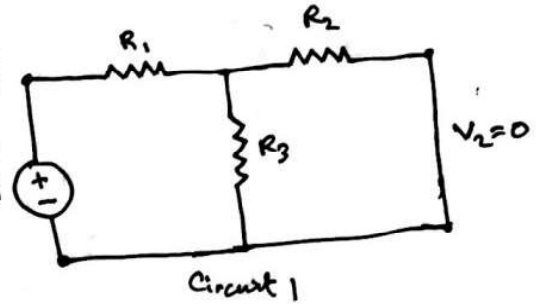
$$V_2 = I_2 R_2 + (I_1 + I_2) R_3 \dots \textcircled{4}$$


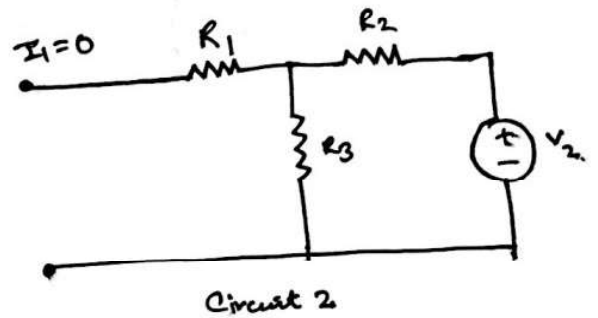
$$\textcircled{3} \Rightarrow V_1 = (R_1 + R_3) I_1 +$$



Inter-relationship

$$[Z] = \begin{bmatrix} z_{11} & z_{12} \\ z_{21} & z_{22} \end{bmatrix}$$

$$[Z] = [Y]^{-1}$$

$$= \begin{bmatrix} Y_{11} & Y_{12} \\ Y_{21} & Y_{22} \end{bmatrix}^{-1}$$

$$= \frac{1}{\Delta Y} \begin{bmatrix} Y_{22} & -Y_{12} \\ -Y_{21} & Y_{11} \end{bmatrix}$$

\downarrow
Determinant

or T-
ABCD Parameters

$$V_1 = AV_2 + B(-I_2) \dots \textcircled{1}$$

$$I_1 = CV_2 + D(-I_2) \dots \textcircled{2}$$

z-parameter

$$V_1 = z_{11}I_1 + z_{12}I_2 \dots \textcircled{3}$$

$$V_2 = z_{21}I_1 + z_{22}I_2 \dots \textcircled{4}$$

$$\textcircled{2} \Rightarrow CV_2 = I_1 + DI_2$$

$$\Rightarrow V_2 = \frac{1}{C}I_1 + \frac{D}{C}I_2 \dots \textcircled{5}$$

Comparing $\textcircled{5}$ and $\textcircled{4}$,

$$z_{21} = \frac{1}{C} \quad z_{22} = \frac{D}{C}$$

Putting $\textcircled{5}$ in $\textcircled{1}$,

$$V_1 = A\left(\frac{1}{C}I_1 + \frac{D}{C}I_2\right) + B(-I_2)$$

$$\Rightarrow V_1 = \frac{A}{C}I_1 + \left(\frac{AD}{C} - B\right)I_2 \dots \textcircled{6}$$


\therefore Comparing $\textcircled{6}$ and $\textcircled{3}$,

$$z_{11} = \frac{A}{C}$$

$$z_{12} = \frac{AD}{C} - B = \frac{AD - BC}{C} = \frac{\Delta T}{C}$$

Determinant of
T matrix
 ΔT


1. Find out all the parameters.

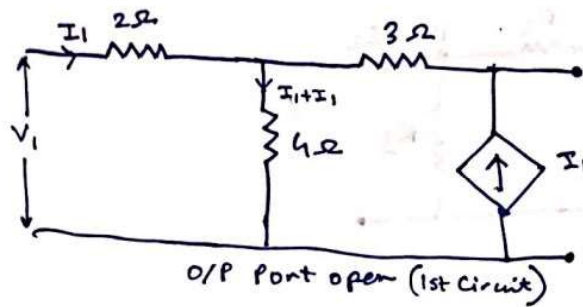

$$V_1 = 2I_1 + 4(2I_1) \dots \textcircled{1}$$


$$\Rightarrow \frac{V_1}{I_1} = 10\Omega = Z_{11}$$

2nd Circuit
Input Port open

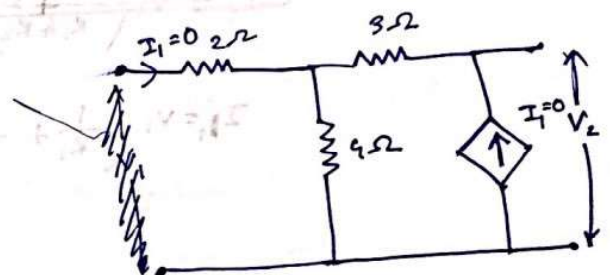

$$V_2 = 3I_1 + 2I_1(4) \dots \textcircled{2}$$
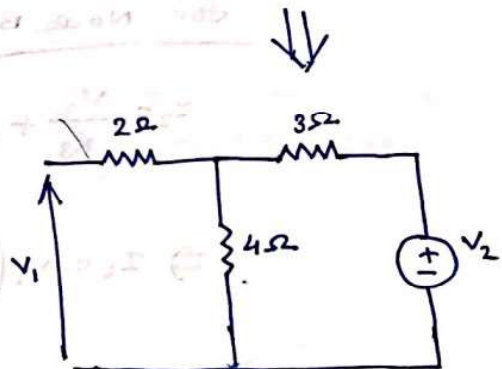
$$\Rightarrow \frac{V_2}{I_1} = Z_{21} = 11\Omega$$



$$V_1 = 4I_2$$


$$\therefore \frac{V_1}{I_2} = 4\Omega = Z_{12}$$

$$V_2 = (3+4)I_2$$

$$\therefore \frac{V_2}{I_2} = Z_{22} = 7\Omega$$

Find all the parameters

2.

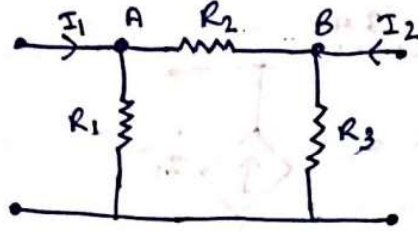

for Node A

$$I_1 = \frac{V_1}{R_1} + \frac{V_1 - V_2}{R_2}$$

$$I_1 = V_1 \left(\frac{1}{R_1} + \frac{1}{R_2} \right) + \left(-\frac{1}{R_2} \right) V_2$$

$$I_1 = V_1 \left(\frac{1}{R_1} + \frac{1}{R_2} \right) + \left(-\frac{1}{R_2} \right) V_2$$

for Node B

$$I_2 = \frac{V_2}{R_3} + \frac{V_2 - V_1}{R_2}$$

$$\Rightarrow I_2 = V_1 \left(-\frac{1}{R_2} \right) + V_2 \left(\frac{1}{R_2} + \frac{1}{R_3} \right)$$

$$\therefore Y_{11} = \frac{1}{R_1} + \frac{1}{R_2}$$

$$Y_{12} = -\frac{1}{R_2}$$



$$Y_{21} = -\frac{1}{R_2}$$

$$Y_{22} = \frac{1}{R_2} + \frac{1}{R_3}$$

Condition of Reciprocity

~~$I_2' = I_1'$~~

$$I_2' = I_1'$$

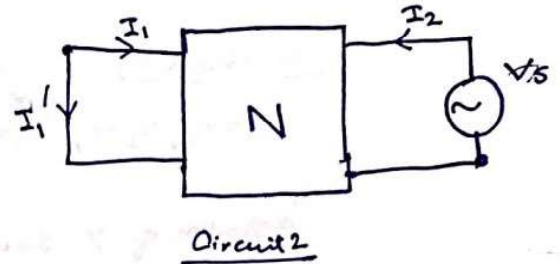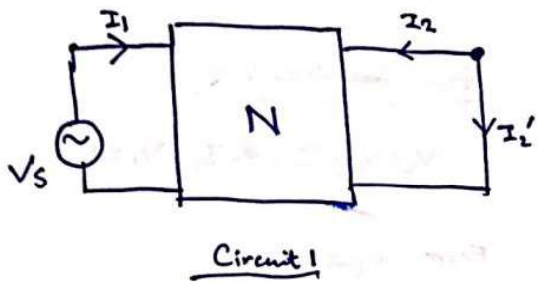

Z parameter

for circuit 1

$$V_1 = V_s; V_2 = 0; I_2' = -I_2$$

definition of z parameter:

$$V_1 = Z_{11}I_1 + Z_{12}I_2 \dots \textcircled{1}$$

$$V_2 = Z_{21}I_1 + Z_{22}I_2 \dots \textcircled{2}$$

From equation ①;

$$V_s = Z_{11}I_1 - Z_{12}I_2' \dots \textcircled{3}$$

From equation ②,

$$0 = Z_{21}I_1 - Z_{22}I_2' \dots \textcircled{4}$$

$$I_2' = \frac{V_s Z_{21}}{Z_{11}Z_{22} - Z_{12}Z_{21}}$$

Now $I_2' = I_1'$

$$\Rightarrow \boxed{Z_{21} = Z_{12}}$$

For ~~for~~ Circuit 2:

$$V_2 = V_s; I_1' = -I_1; V_1 = 0$$

From equation ①,

$$0 = -Z_{11}I_1' + Z_{12}I_2 \dots \textcircled{5}$$

From equation ②,

$$V_s = -Z_{21}I_1' + Z_{22}I_2 \dots \textcircled{6}$$

$$I_1' = \frac{V_s Z_{12}}{Z_{11}Z_{22} - Z_{21}Z_{12}}$$

Y Parameter

for circuit 1,

$$V_1 = V_s; V_2 = 0; I_2' = -I_2$$

definition of Y parameter:

$$I_1 = Y_{11}V_1 + Y_{12}V_2 \dots \textcircled{1}$$

$$I_2 = Y_{21}V_1 + Y_{22}V_2 \dots \textcircled{2}$$

From equation ①,

$$I_1 = Y_{11}V_s \dots \textcircled{3}$$

From equation ②,

$$I_2' = -Y_{12}V_s \dots \textcircled{4}$$

$$I_2' = -Y_{12}V_s$$

$$\therefore \boxed{Y_{12} = Y_{21}}$$

ABCD Parameter (T Parameter)

for circuit 1,

$$V_1 = V_s; V_2 = 0; I_2' = -I_2$$

definition of T parameter:

$$V_1 = AV_2 - BI_2 \dots \textcircled{1}$$

$$I_1 = CV_2 - DI_2 \dots \textcircled{2}$$

From eq ①,

$$V_s = +BI_2'$$

$$\Rightarrow I_2' = \frac{V_s}{B}$$

$$\therefore \frac{V_s}{B} = \left(\frac{AD - BC}{B} \right) V_s$$
$$\Rightarrow AD - BC = 1$$

$$\boxed{AD - BC = 1}$$

for circuit 2,

$$V_2 = V_s; I_1' = -I_1; V_1 = 0$$

From equation ①,

$$I_1' = (-Y_{12}V_s)$$

for circuit 2,

$$V_2 = V_s; I_1' = -I_1; V_1 = 0$$

From equation ①,

$$0 = AV_s - BI_2'$$

From equation ②,

$$-I_1' = CV_s - DI_2'$$

$$I_1' = \frac{DAV_s}{B} - CV_s$$

$$= V_s \left(\frac{AD}{B} - C \right)$$

$$= V_s \left(\frac{AD - BC}{B} \right)$$

h Parameter

for circuit 1,

$$V_1 = V_S; V_2 = 0; I_2' = -I_2$$


definition of h parameter:

$$V_1 = h_{11} I_1 + h_{12} V_2 \dots \dots \textcircled{1}$$

$$I_2' = h_{21} I_1 + h_{22} V_2 \dots \dots \textcircled{2}$$

HW

Condition of ~~Selection~~ Symmetry $\left(\frac{V_S}{I_1} = \frac{V_S}{I_2} \right)$

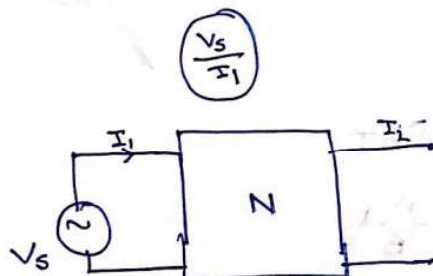

Circuit 1

$$V_1 = V_S; I_2 = 0$$

Z-parameter:


$$V_1 = Z_{11} I_1 + Z_{12} I_2 \dots \dots \textcircled{1}$$

$$V_2 = Z_{21} I_1 + Z_{22} I_2 \dots \dots \textcircled{2}$$

$$V_S = Z_{11} I_1$$

$$\frac{V_S}{I_1} = Z_{11}$$

$$\therefore Z_{11} = Z_{22}$$

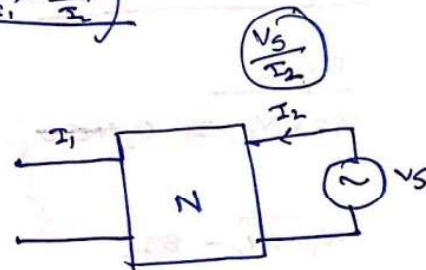

Circuit 2

$$V_2 = V_S; I_1 = 0$$

From equation $\textcircled{2}$,

$$V_S = Z_{22} I_2$$

$$\Rightarrow \frac{V_S}{I_2} = Z_{22}$$

Y-Parameter:

Circuit 1

$$V_1 = V_S, V_2 = 0, \text{ ~~I_1 = 0~~ } I_1 = 0$$

$$I_1 = Y_{11}V_1 + Y_{12}V_2 \dots \text{--- (1)}$$

$$I_2 = Y_{21}V_1 + Y_{22}V_2 \dots \text{--- (2)}$$

$$\Rightarrow \cancel{I_2} = \cancel{Y_{21}V_1} + \cancel{Y_{22}V_2}$$

$$\Rightarrow \cancel{I_2}$$

$$\therefore I_1 = Y_{11}V_1 = Y_{11}V_S$$

$$\Rightarrow \frac{V_S}{I_1} = \frac{1}{Y_{11}}$$

$$\boxed{Y_{11} = Y_{22}}$$

Circuit 2

$$V_2 = V_S, V_1 = 0, I_1 = 0$$

$$\therefore I_2 = Y_{22}V_2$$

$$\Rightarrow I_2 = Y_{22}V_S$$

$$\Rightarrow \frac{V_S}{I_2} = \frac{1}{Y_{22}}$$

ABCD Parameter:

$$\boxed{A = D}$$

Circuit 1

$$V_1 = V_S; I_1 = 0; \text{ ~~V_2 = 0~~ }$$

$$V_1 = AV_2 - BI_2$$

$$I_1 = CV_2 - DI_2$$

$$V_S = BI_2$$

$$I_1 = DI_2$$

$$\text{or, } V_S = \frac{B}{D}I_1$$

$$\Rightarrow \frac{V_S}{I_1} = \frac{B}{D}$$

$$\therefore \frac{B}{D} = \frac{B}{A}$$

$$\Rightarrow \boxed{A = D}$$

$$0 = AV_S + BI_2$$

$$\Rightarrow I_2 = \frac{A}{B}V_S$$

$$\Rightarrow \frac{V_S}{I_2} = \frac{B}{A}$$

h Parameters

$$h_{11}h_{22} - h_{21}h_{12} = 1$$

$$V_1 = h_{11}I_1 + h_{12}V_2$$

$$I_2 = h_{21}I_1 + h_{22}V_2$$

Circuit 1,

$$V_S = h_{11}I_1 + 0$$

$$I_2 = h_{21}I_1 + 0$$

$$\text{or, } \frac{V_S}{I_1} = h_{11}$$

Circuit 2

$$0 = h_{11}I_1 + h_{12}V_S$$

$$I_2 = h_{21}I_1 + h_{22}V_S$$


$$\Rightarrow I_2 = -\frac{h_{21}h_{12}}{h_{11}} + h_{22}V_S$$

$$\Rightarrow I_2 = V_S \left(\frac{-h_{21}h_{12} + h_{11}h_{22}}{h_{11}} \right)$$

$$\Rightarrow \frac{V_S}{I_2} = \frac{h_{11}}{h_{11}h_{22} - h_{21}h_{12}}$$

$$\Rightarrow h_{11}h_{22} - h_{21}h_{12} = 1$$

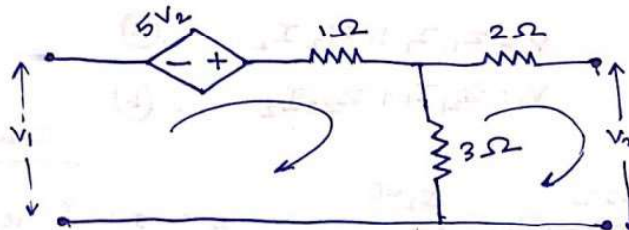1. Find if the network is reciprocal or not, and symmetric or not.



in ~~the~~ Loop ①,

$$V_1 + 5V_2 = I_1 + (I_1 + I_2)3$$

$$V_2 = 2I_2 + (I_2 + I_1)3$$

$$\text{or, } V_1 + 5V_2 = 4I_1 + 3I_2$$

$$\text{or, } V_2 = 3I_1 + 5I_2$$

$$\text{or, } V_1 = 4I_1 - 15I_1 + 3I_2 - 25I_2$$

$$\text{or, } V_1 = -11I_2 - 22I_2$$

$$V_2 = 3I_1 + 5I_2$$

$$V_1 = Z_{11}I_1 + Z_{12}I_2$$


$$V_2 = Z_{21}I_1 + Z_{22}I_2$$

$$Z_{11} = -11$$

$$Z_{12} = -24$$

$$Z_{21} = 3$$

$$Z_{22} = 5$$

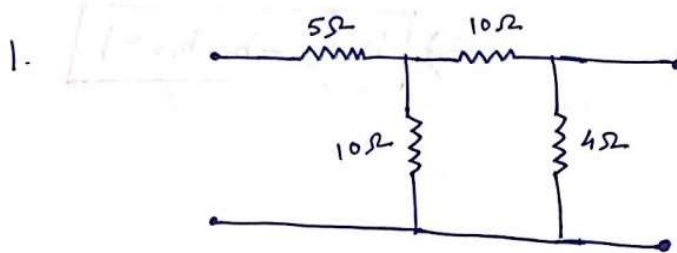



i) Determine Z parameters

ii) Check whether the network is reciprocal.

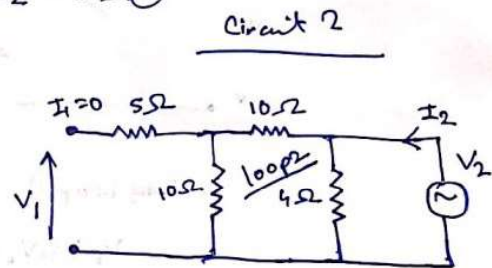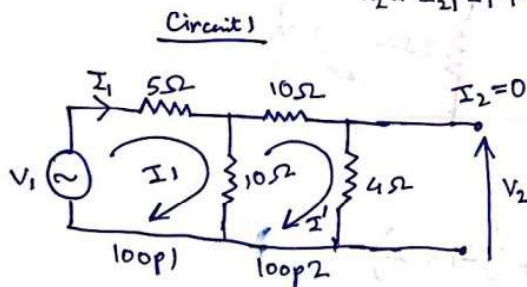iii) Check whether the network is symmetric.

$$V_1 = Z_{11}I_1 + Z_{12}I_2 \dots \textcircled{a}$$

$$V_2 = Z_{21}I_1 + Z_{22}I_2 \dots \textcircled{b}$$



For loop 2:

$$10I' + 4I' + 10(I' - I) = 0$$

$$\Rightarrow 24I' = 10I_1 \dots \textcircled{1} \Rightarrow I' = \frac{10}{24}I_1$$

For loop 1:

$$V_1 = 5I_1 + 10(I_1 - I') \dots \textcircled{2}$$

$$\Rightarrow \frac{V_1}{I_1} = 10.83\Omega = Z_{11}$$

$$Z_{11} = \left. \frac{V_1}{I_1} \right|_{I_2=0}$$

$$Z_{12} = \left. \frac{V_1}{I_2} \right|_{I_1=0}$$

$$Z_{21} = \left. \frac{V_2}{I_1} \right|_{I_2=0}$$

$$Z_{22} = \left. \frac{V_2}{I_2} \right|_{I_1=0}$$

$$\therefore \text{Now, } V_2 = 4I' = \frac{10}{24} \times 4 \times \left(\frac{10}{24} I_1 \right) \left[\because I' = \frac{10}{24} I_1 \right]$$

$$\therefore \frac{V_2}{I_1} = \frac{10}{6} = 1.67 \Omega = Z_{21}$$

From Circuit 2

From loop 2

$$10I'' + 10I'' + 4I'' - 4I_2 = 0$$

$$\Rightarrow 24I'' = 4I_2 \dots \dots \textcircled{3}$$

$$I_2 = \frac{V_2}{\frac{4 \times 20}{4 + 20}}$$

$$\therefore \frac{V_2}{I_2} = \frac{80}{24} = \frac{10}{3} = 3.33 \Omega$$

$$V_1 = 10I'' = 10 \left(\frac{4}{24} \right) I_2$$


$$\therefore \frac{V_1}{I_2} = \frac{10}{6} \left(\frac{4}{24} \right) I_2$$

$$\therefore \frac{V_1}{I_2} = \frac{10}{6} = 1.67 \Omega$$


$$= Z_{12}$$

$$\therefore \begin{bmatrix} z_{11} & z_{12} \\ z_{21} & z_{22} \end{bmatrix} = \begin{bmatrix} 10.83 & 1.67 \\ 1.67 & 3.77 \end{bmatrix} \quad (92)$$

2.

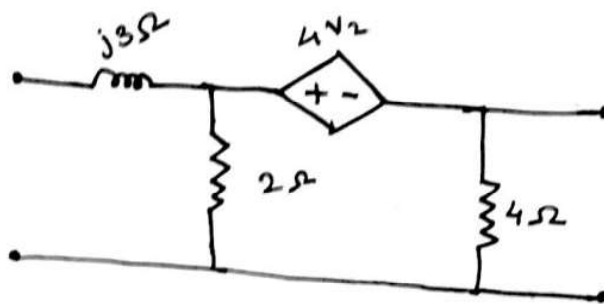

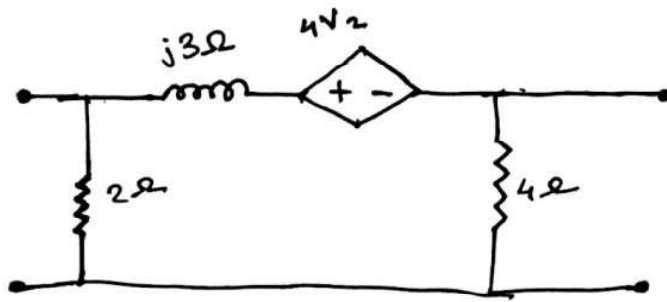1. i) Determine z parameter
 ii) Y parameter
 iii) ABCD Parameter
 iv) h -parameter
2. Check the condition of reciprocity
3. Check the condition of symmetry



$$Y_{11} = \left(\frac{1}{2} + \frac{1}{j3} \right)$$

$$Y_{12} = -\frac{5}{j3}$$

$$Y_{21} = -\frac{1}{j3}$$

$$Y_{22} = \frac{5}{j3} + \frac{1}{2}$$