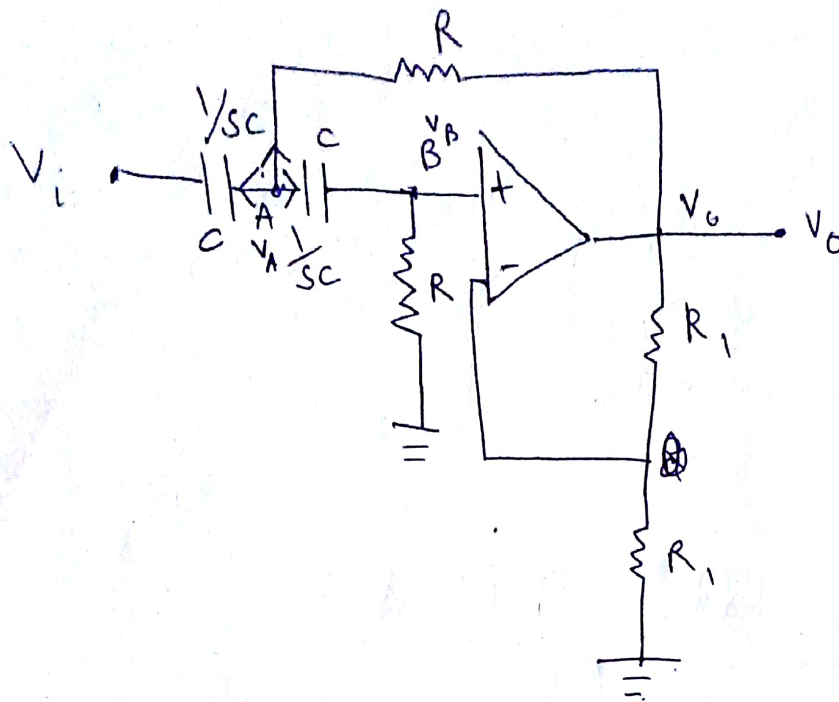


## 2nd Order HPF:-



2nd order HPF contain 2 storage elements

like capacitor, It has a very high and constant gain where the signal level is very high compared to the 1st order HPF. When the frequency is <sup>low</sup> the gain of filter is very low compared to 1st order. The frequency response is better in second order HPF as compared to 1st order.

Apply KCL at node A,

[Assuming potential higher at A than other pts].

$$\frac{V_A - V_i}{\frac{1}{sC}} + \frac{V_A - V_o}{R} + \frac{V_A - V_B}{\frac{1}{sC}} = 0$$

$$\Rightarrow V_A \left( SC + \frac{1}{R} \right) - SC V_i - SC V_B \quad \text{--- (3)}$$

$$\frac{V_0 - V_B}{R_1} = \frac{V_B - 0}{R_1}$$

$$\Rightarrow V_B = \frac{V_0}{2} \quad \text{--- (2)}$$

$$\frac{V_A - V_B}{\frac{1}{SC}} = \frac{V_B}{R}$$

$$\Rightarrow SC V_A = V_B \left( SC + \frac{1}{R} \right)$$

$$\Rightarrow SC V_A = \frac{V_0}{2} \left( SC + \frac{1}{R} \right)$$

$$\Rightarrow V_A = \frac{V_0}{2} \left( \frac{SC R + 1}{SC R} \right) \quad \text{--- (1)}$$

From 3

$$\begin{aligned} & \frac{V_0}{2} \left( \frac{SC R + 1}{SC R} \right) \left( \frac{SC R + 1}{R} \right) - SC \frac{V_0}{2} \\ & - SC \frac{V_0}{2} - \frac{V_0}{R} = 0 \end{aligned}$$

$$\Rightarrow \frac{V_o}{SCR} (SCR+1)(2SCR+1)$$

$$-2CRV_i - SCR V_o - 2V_o = 0,$$

$$\Rightarrow \frac{V_o}{SCR} (2S^2C^2R^2 + 3SCR + 1)$$

$$-2SCR V_i - SCR V_o - 2V_o = 0,$$

$$\Rightarrow V_o (2S^2C^2R^2 + 3SCR + 1)$$

$$-2S^2C^2R^2 V_i - SCR^2 V_o - 2V_o SCR = 0,$$

$$\Rightarrow SCR^2 V_o + V_o SCR + V_o - 2S^2C^2R^2 V_i = 0,$$

$$\Rightarrow \frac{V_o}{V_i} = \frac{2S^2C^2R^2}{S^2C^2R^2 + SCR + 1}$$

$$H(s) = \frac{2S^2}{S^2 + \frac{S}{RC} + \left(\frac{1}{RC}\right)^2}$$



$$H(s) = \frac{2s^2}{s^2 + \frac{s}{RC} + \left(\frac{1}{RC}\right)^2}$$


$$= \frac{Ks^2}{s^2 + \left(\frac{\omega_0}{2}\right)s + (\omega_0)^2}$$

$$K=2$$

$Q \rightarrow$  quality factor or fig. of merit.

$$\frac{V_o}{V_i} = \frac{k}{1 + \frac{\omega_0}{s} + \left(\frac{\omega_0}{s}\right)^2}$$

Case 1 :-  $\omega \ll \omega_0$

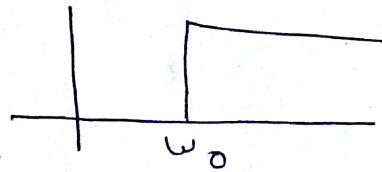

$$\frac{V_o}{V_i} = \frac{k}{1 + \frac{\omega_0}{j\omega} + \left(\frac{\omega_0}{j\omega}\right)^2} \rightarrow 0$$

Case 2 :-  $\omega_0 \ll \omega$

$$\frac{V_o}{V_i} = k \Rightarrow V_o = k V_i$$

Conclusion - (i) From this experiment,  
it is said that the presence of  $s^2$  in  
numerator, makes the active filter very  
high & const gain  
at very high frequency.

(ii) At low frequency,  $\omega \ll \omega_0$ ,

$$V_o \rightarrow 0, \quad \frac{V_o}{V_i} \rightarrow 0$$

i.e. filter drops low frequency signal  
to reach output.

(iii) Cut off frequency  $\omega_0$  depends on R &  
C values. By varying R & C  $\omega_0$  can  
be changed.



Q in this exp = 1

as here resistor & capacitor  
are chosen with identical values

Q depends on R & C values  
while changing R & C, Q can be  
changed.






## Pattern of Response:-

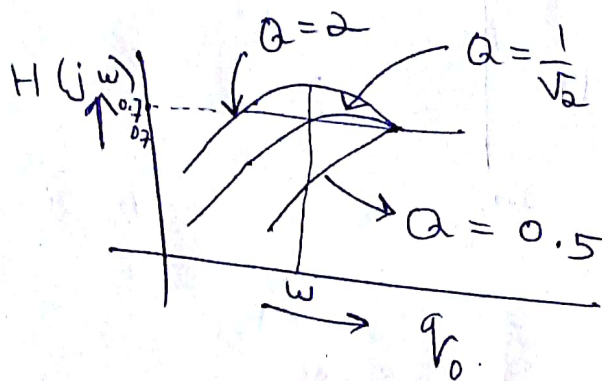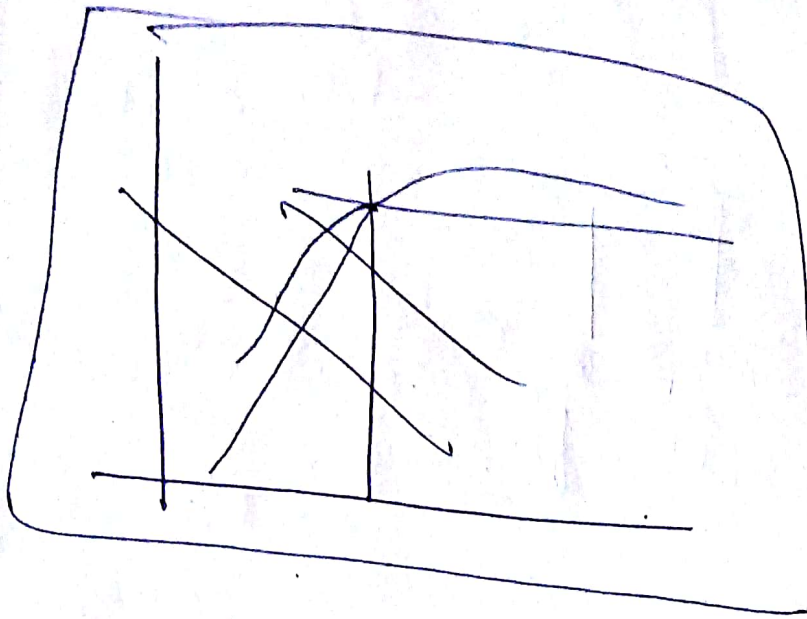


By adjusting value of  $R$  &  $C$  value of  $Q$  can be adjusted to have different pattern of response. At  $Q = \frac{1}{\sqrt{2}}$  i.e. 0.707, the extension of the horizontal portion of response towards cut off is max flat which is most desired response of the second order H.P.F.



# 1st order BPF

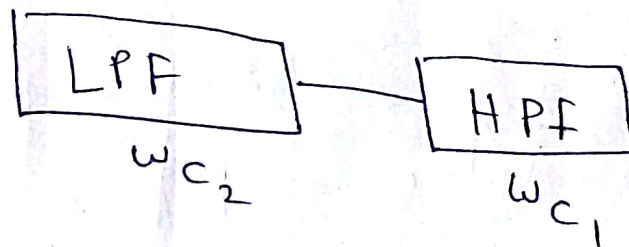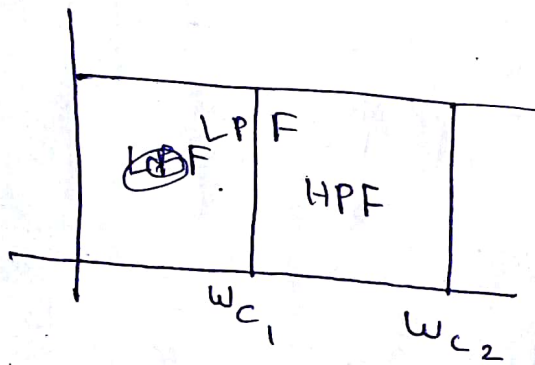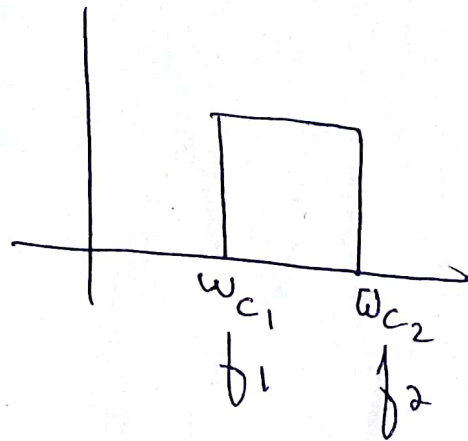

$$\omega_{c1} < \omega_{c2}$$

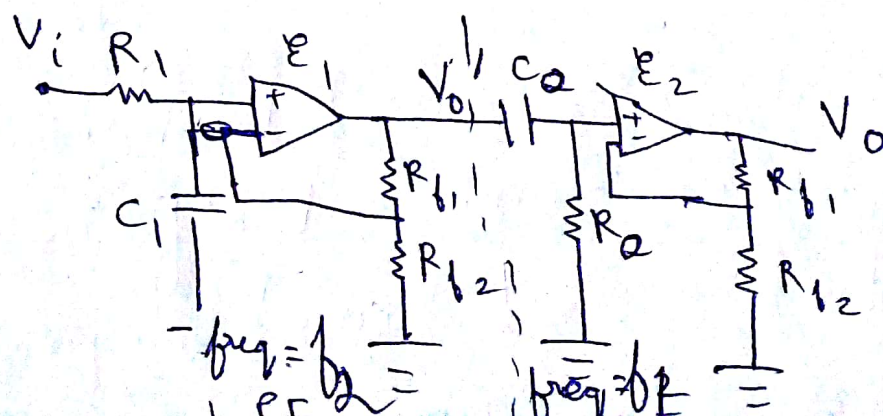

$$f_2 > f_1$$

$$f_2 - f_1 = \text{Bandwidth:-}$$

$$f_2 = \frac{1}{2\pi R_1 C_1}$$

$$f_1 = \frac{1}{2\pi R_0 C_0}$$

$$\frac{V_o}{V_i} = \frac{V_o}{V_o'} \times \frac{V_o'}{V_i}$$

$$= \cancel{A} \left[ \frac{1}{\sqrt{1 + \left(\frac{\omega_0}{\omega}\right)^2}} \right] \times \cancel{A} \left[ \frac{1}{\sqrt{1 + \left(\frac{\omega}{\omega_0}\right)^2}} \right]$$

$$= \frac{s C_0 R_0}{1 + s C_0 R_0} \times \frac{1}{1 + s C_1 R_1}$$


$$= \frac{s C_0 R_0}{1 + s(C_0 R_0 + C_1 R_1) + s^2 R_1 C_1 R_0 C_0}$$

$$= \frac{s C_0 R_0}{R_0 C_0 R_1 C_1 \left[ s^2 + \frac{s}{R_1 C_1} + \frac{s}{R_0 C_0} + \frac{1}{R_1 C_1 R_0 C_0} \right]}$$




$$\Rightarrow \frac{V_o}{V_i} = \frac{S}{R_1 C_1 \left[ S^2 + \frac{S}{R_1 C_1} + \frac{S}{R_2 C_2} + \frac{1}{R_1 C_1 R_2 C_2} \right]}$$
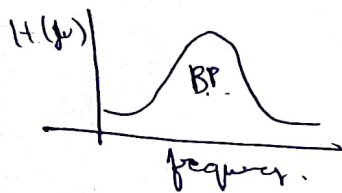
$$H(j\omega) = \frac{S \omega_c^2}{S^2 + S(\omega_c^2 + \omega_{c1}) + \omega_c^2 \omega_{c1}}$$



$$\frac{1}{R_1 C_1} = \omega_{c1}$$

Band Reject Filter -

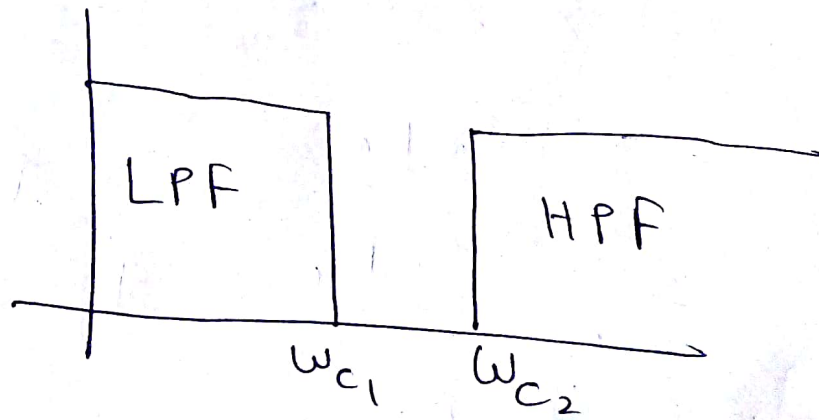

$$\omega_{c2} > \omega_{c1}$$

cut off freq. of HPF > cut off  
freq. of LPF

