

G-A

(i) (i) (a) non-linear circuits

(ii) (c) equivalent voltage source and impedance in series.

(iii) (b) capacitive (Not sure)

(iv) (a) 0 $\left[\lim_{s \rightarrow \infty} sF(s) \right]$

(v) (b) frequency domain response only

(vi) (d) All of the above


(vii)

(viii) (d) $AD - BC > 1$

(ix) (d) ΔA or ΔB

(x) (d) $R = 0$.

Group-B

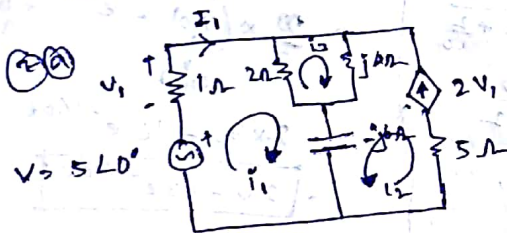

∴ From KVL

$$5\angle 0^\circ = I_1 \times 1 + 2(I_1 - I_3) + (-j6)(I_1 + I_2)$$

$$\boxed{I_2 = 2}$$

$$2(I_3 - I_1) + j4(I_3 + I_2) = 0$$

$$\Rightarrow 2I_3 - 2I_1 + j4I_3 + j8 = 0$$

$$\Rightarrow \boxed{-2I_1 + I_3(2 + j4) = -j8}$$

$$5\angle 0^\circ + j10 = I_1 + 2I_1 - 2I_3 - j6I_1 - j12$$

$$\Rightarrow 5 = I_1(3 + j6) - 2I_3 + j12$$

$$\Rightarrow \boxed{(3 + j6)I_1 - 2I_3 = 5 + j12}$$

$$\therefore \begin{bmatrix} -2 & 2 + j4 \\ 3 + j6 & -2 \end{bmatrix} \begin{bmatrix} I_1 \\ I_3 \end{bmatrix} = \begin{bmatrix} -j8 \\ 5 + j12 \end{bmatrix}$$

$$\begin{aligned}
 \Delta A &= (-2)(-2) - (2+j4)(3+j6) \\
 &= 4 - (6 + j^2 24 + 12j + 12j) \\
 &= 4 - 6 + 24 + 24j \\
 &= \boxed{22 + 24j}
 \end{aligned}$$

$$A_1 = \begin{vmatrix} -j8 & 2+j4 \\ 5+j12 & -2 \end{vmatrix}$$

$$\begin{aligned}
 A_1 &= 16j - (2+j4)(5+j12) \\
 &= 16j - (10 + 24j + 20j - 48) \\
 &= 16j - 10 - 44j + 48 \\
 &= \boxed{38 - 28j}
 \end{aligned}$$

$$\therefore i_1 = \frac{38 - 28j}{22 + 24j} = \boxed{\frac{19 - 14j}{11 + 12j}}$$

\therefore Current through $-j6\Omega$ is i_1 and i_2


$$= \frac{19 - 14j}{11 + 12j} + 2$$

$$= \frac{19 - 14j + 22 + 24j}{11 + 12j}$$

$$= \boxed{\frac{41 + 10j}{11 + 12j}}$$

$$\begin{array}{r} 44 \\ 16 \\ \hline 28 \end{array}$$

Q24

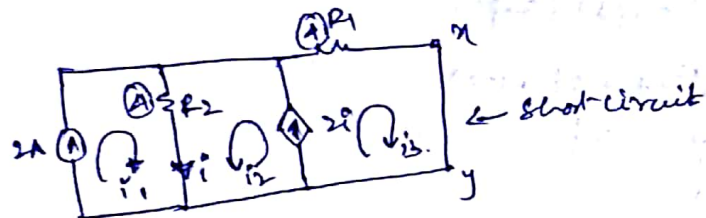


In loop 1,

$$i_1 = 2A$$

In loop 2,

$$i_2 = 2i$$

$$i_1 + i_2 = i$$

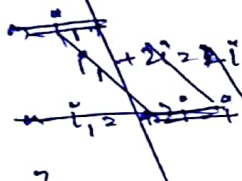


$$i_1 = i - 2i = -i$$

$$i = -2$$


For loop 3,

$$i_3 = -4A$$

For R1,

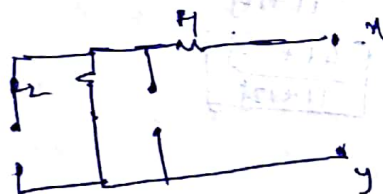

$$\therefore R_{th} = 4 + 4 = 8\Omega$$

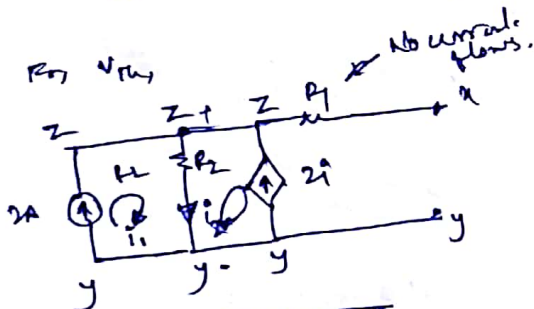

$$V_{th} = (V_x - V_z) + (V_z - V_y)$$

$$\therefore V_z = V_x$$

$$V_{th} = i R_2$$


$$i_1 = 2A, i_2 = 2i$$

$$i_1 + i_2 = i$$

$$\therefore i = 2 + 2i$$

$$\therefore i = -2A$$

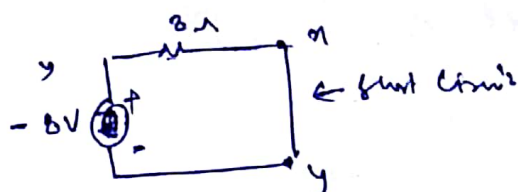
$$\therefore V_{th} = -2 \times 4 = -8V$$





$$\therefore I = \frac{-8}{8} = -1A$$

$$\text{from } y \text{ to } x$$

Q333

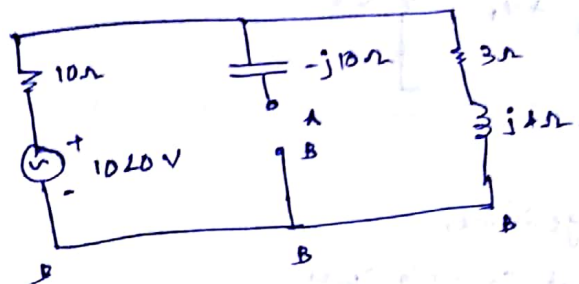


For R_{th} ,

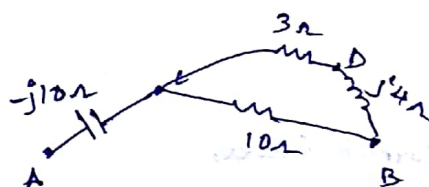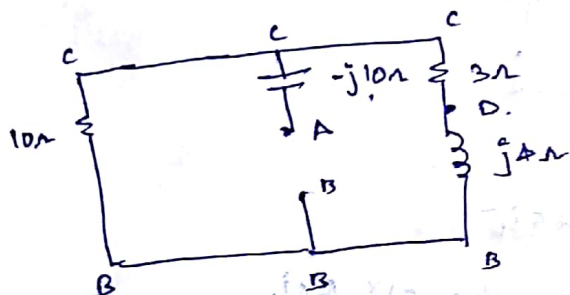

$$\begin{aligned}
 \therefore R_{eq} &= -j10\Omega + \frac{(3\Omega + j4\Omega) \times (10\Omega)}{10\Omega + 3\Omega + j4\Omega} \\
 &= -j10\Omega + \frac{30 + j40}{13 + j4} \\
 &= \frac{-j130 + 40 + 30 + j40}{13 + j4} \\
 &= \boxed{\frac{70 - j90}{13 + j4}} \text{ (Ans)}
 \end{aligned}$$


Now, for V_{th} ,

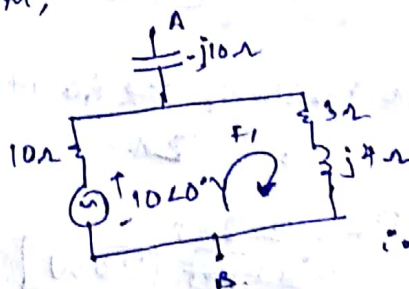

$$I_1 = \frac{10}{13 + j4}$$

$$\begin{aligned}
 \therefore V_{AB} &= 10 - 10 \times \frac{10}{13 + j4} \\
 &= 10 - \frac{100}{13 + j4} \\
 &= \boxed{\frac{30 + j40}{13 + j4}} \text{ (Ans)}
 \end{aligned}$$

(A) (B) (C)

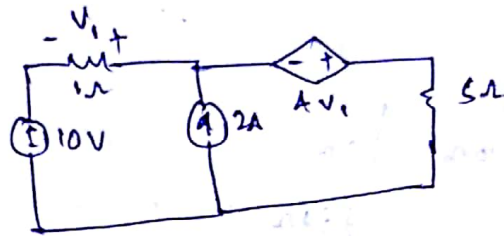

Now, Using only Voltage Source,
Current Source is open
circuited.



~~10 = 10~~

$$10 = i_1 \times 1 - \Delta V_1 + 5i_1$$

a $10 = 6i_1 - \Delta V_1$ Now, $V_1 = -1 \times \Delta i_1$


a $10 = 6i_1 + 4i_1$ $= -i_1$

$\Rightarrow \boxed{i_1 = 1A}$

(B)

V_1

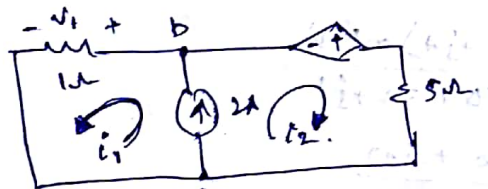Now, with only ~~Voltage~~ Current Source,



~~$i_1 = 2A$~~ $\boxed{i_1 + i_2 = 2A}$

$V_{ba} = V_1$ (From the figure)

$= \boxed{1A}$

c. $V_1 + \Delta V_1 = 5i_2$

$\Rightarrow 5V_1 = 5i_2$

~~$i_2 = V_1 = 2A$~~ $5i_1 = 5i_2 \Rightarrow \boxed{i_1 = i_2 = 2/2 = 1A}$

c. total Current through 5Ω resistor is ~~1A~~ $1+1$
 $= 2A$

c. Power $= i^2 R = \cancel{2 \times 2 \times 5}$ $\boxed{20W}$

Group - C:

(Q.1) (a) 'Gate' signal is a type of signal which restricts the function within a bound (say from T_1 to T_2) when represented in time domain the gate signal is defined as,

$$G_{T_1, T_2} = \begin{cases} a & T_1 \leq T \leq T_2 \\ 0 & \text{otherwise} \end{cases}$$

(constant if $a=1$ the unit gate signal)

Alternatively, gate signal is also defined as,

$$G_{T_1, T_2} = u(t - T_1) - u(t - T_2)$$

where $u(t)$ is a step function.

Ramp function is defined as


$$r(t) = \begin{cases} t & t \geq 0 \\ 0 & \text{otherwise} \end{cases}$$

Also, delay time is T

$$\therefore r(t) = \begin{cases} t - T & t \geq T \\ 0 & \text{otherwise} \end{cases}$$



(Q.2) (a)

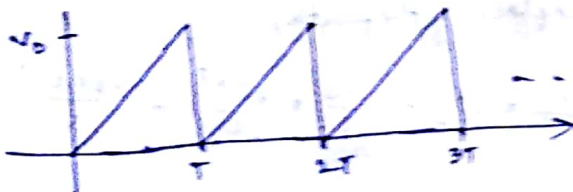

from the figure we can see that the time period of the function is T

\therefore we can find the fundamental period and then find for the whole function.



Now, the equation is,

$$y = mx + c$$

$$\therefore f(t) = \frac{v_0}{T} t + 0 \quad [\text{intercept} = 0]$$

$$\therefore \boxed{f(t) = \frac{v_0}{T} t}$$

~~is equal function is, f(t)~~

$$\therefore F(s) = \mathcal{L}\{f(t) \cdot g(0, T)\}$$

$$= \mathcal{L}\{f(t) (u(t) - u(t-T))\}$$

$$= \mathcal{L}\left\{\frac{v_0}{T} t u(t) - \frac{v_0}{T} t u(t-T)\right\}$$

~~$$\frac{v_0}{T} t u(t)$$~~

$$\therefore F(s) = \frac{v_0}{T} \times \mathcal{L}\{t u(t)\} - \frac{v_0}{T} \times \mathcal{L}\{(t-T+T)u(t-T)\}$$

$$= \frac{v_0}{T} \times \frac{1}{s^2} - \frac{v_0}{T} \times (\mathcal{L}\{(t-T)u(t-T)\} + \mathcal{L}\{T u(t-T)\})$$

$$= \frac{v_0}{T} \times \frac{1}{s^2} - \left(\frac{v_0}{T} \times \frac{e^{-sT}}{s^2} + \frac{v_0}{T} \times T \times \frac{e^{-sT}}{s} \right)$$

$$= \boxed{\frac{v_0}{T} \times \frac{1}{s^2} - \frac{v_0}{T} \times \frac{e^{-sT}}{s^2} - \frac{v_0}{s} e^{-sT}}$$

~~$$= \frac{v_0}{s} \left(\frac{1}{sT} - \right)$$~~

Now, for the whole Laplace of the function,

$$F(s) = \left(\frac{v_0}{T} \times \frac{1}{s^2} - \frac{v_0}{T} \times \frac{e^{-sT}}{s^2} - \frac{v_0 e^{-sT}}{s} \right) \times \frac{1}{1-e^{-sT}}$$

multiplication

(A).

②④② Impulse function is a function $\delta(t)$ which is defined as:-

$$\delta(t) = \begin{cases} \infty & t=0 \\ 0 & \text{otherwise.} \end{cases}$$

So, the value is ∞ at $t=0$ and 0 otherwise.

~~if $\delta(t)=0$ then it is known as unit impulse function.~~

unit step function $= u(t) = \begin{cases} 1 & t \geq 0 \\ 0 & \text{otherwise.} \end{cases}$

Now, $L\{u(t)\} = L\{1\}$
 $= \frac{1}{s}$

Now, $L\left\{\frac{du(t)}{dt}\right\} = s \times L\{u(t)\}$ [$u(0)=0$]
 $= s \times \frac{1}{s} = 1$



equal to the Laplace of impulse function

$$\begin{aligned} L\{\delta(t)\} &= \int_{0^-}^{\infty} \delta(t) e^{-st} dt \\ &= \int_{0^-}^{0^+} \delta(t) e^{-st} dt \\ &= \left[\text{Now acc. to shifting property.} \right. \\ &\quad \left. \int_{0^-}^{0^+} \delta(t) f(t) dt = f(0) \right] \end{aligned}$$


$$\therefore L\{\delta(t)\} = e^{-s \cdot 0} = 1$$

Hence Proved

(15a)

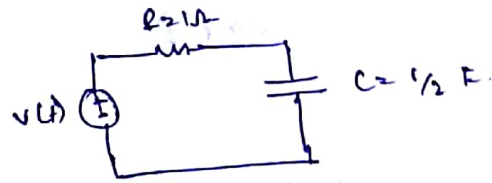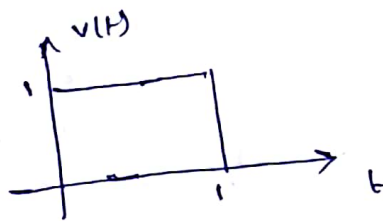

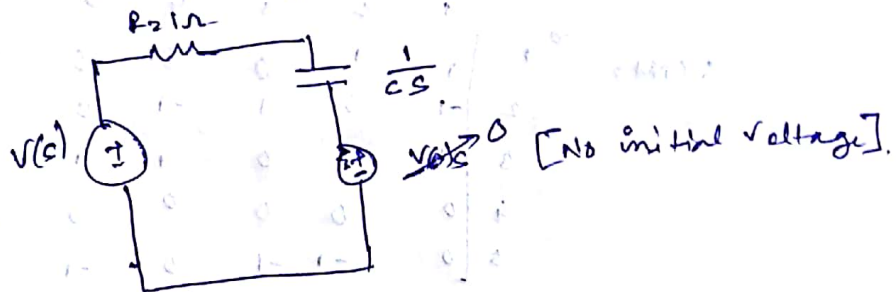Now, Converting the Circuit to s-domain, we get



∴ Circuit is,



$$\begin{aligned} \text{Now, } V(s) &= \mathcal{L}\{u(t) - u(t-1)\} \\ &= \mathcal{L}\{u(t)\} - \mathcal{L}\{u(t-1)\} \\ &= \frac{1}{s} - \frac{e^{-s}}{s} \end{aligned}$$

Now, Applying KVL, we get,

$$\begin{aligned} V(s) &= I(s) \times 1 + \frac{2}{s} \times I(s) \\ \therefore I(s) &= \frac{V(s)}{1 + 2/s} = \frac{\frac{1}{s} - \frac{e^{-s}}{s}}{1 + \frac{2}{s}} \\ &= \frac{1 - e^{-s}}{s + 2} \end{aligned}$$

$$I(s) = \frac{1}{s+2} - \frac{e^{-s}}{s+2}$$


$$\begin{aligned} \therefore i(t) &= \mathcal{L}^{-1}\{I(s)\} \\ &= \mathcal{L}^{-1}\left\{\frac{1}{s+2}\right\} - \mathcal{L}^{-1}\left\{\frac{e^{-s}}{s+2}\right\} \\ &= e^{-2t} - e^{-2(t-1)} u(t-1) \end{aligned}$$

$$i(t) = e^{-2t} - e^{-2(t-1)} u(t-1) \quad (A)$$

$$e^{-2t} - e^{-2(t-1)} u(t-1)$$

Group-D


(1) (b) (a)

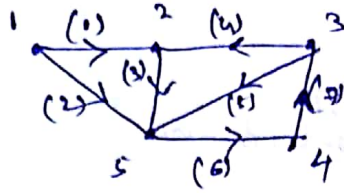

∴ CM1 =

$$\begin{bmatrix} 1 & 2 & 3 & 4 & 5 & 6 & 7 \\ 1 & 1 & 0 & 0 & 0 & 0 & 0 \\ 2 & -1 & 0 & 1 & -1 & 0 & 0 \\ 3 & 0 & 0 & 0 & 1 & 0 & -1 \\ 4 & 0 & 0 & 0 & 0 & -1 & 1 \\ 5 & 0 & -1 & -1 & 0 & 1 & 0 \end{bmatrix}$$

(b)

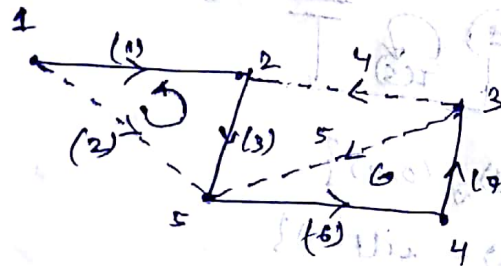


∴ Tie-set =

$$\begin{bmatrix} 1 & 2 & 3 & 4 & 5 & 6 & 7 \\ 2 & -1 & 1 & -1 & 0 & 0 & 0 \\ 4 & 0 & 0 & 1 & 1 & 0 & 1 \\ 5 & 0 & 0 & 0 & 1 & 1 & 1 \end{bmatrix}$$

cutset 2
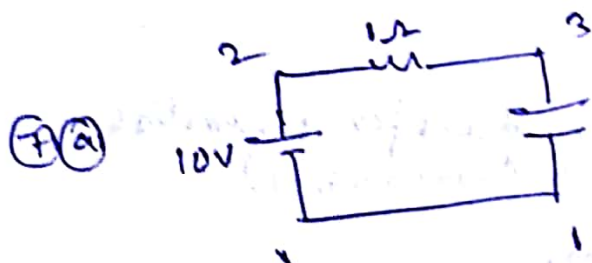
$$\begin{bmatrix} 1 & 2 & 3 & 4 & 5 & 6 & 7 \\ 3 & 1 & 0 & 0 & 0 & 0 & 0 \\ 6 & 0 & 1 & 0 & 0 & 0 & 0 \\ 7 & 0 & 0 & 1 & 0 & 0 & 0 \end{bmatrix}$$



$$Z = R = 0.5$$

$$Z_1 = 0.5 / 10 = 0.05$$

$$Z_2 = 0.5 \times 10 = 5$$

Plot

N	2	1
R	2	3
C	3	1

DC 10

0.5

0.05

5

VIC

• PLOT TRAN
• END

(17b)

• Port 1 - Port tells Pspice to print the values in the form of a table.

• PRINT (output variable)
↓
gets printed.

• Plot 1 - Plot tells Pspice to plot the output variable in a graph.

• AC - Tells Pspice to vary the freq. of AC in the circuit.

• AC dc → Vary in the form of decads
 Lin → Vary linearly
 Oct → Vary in powers of 2

(18a)

(18a) ABCD parameters also known as transfer parameters (transmission)

are the parameters defined as,

V_1 and I_1 are considered dependent

whereas V_2 and I_2 are considered independent.

These parameters provide a measure of how a circuit transmits voltage or current from source to load.

$$\begin{cases} V_1 = A I_2 - B I_2 \\ I_1 = C V_2 - D I_2 \end{cases}$$


A = Open-circuit voltage ratio ($I_2 = 0$)

C = Negative open-circuit transfer admittance ($I_2 = 0$)

B = Negative short-circuit transfer impedance ($V_2 = 0$)

D = Negative short-circuit current ratio ($V_2 = 0$)

(1) (b)

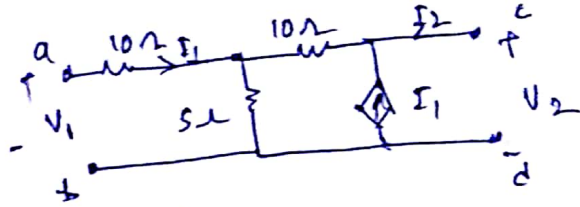


$$\therefore V_1 = Z_{11} I_1 + Z_{12} I_2$$

$$V_2 = Z_{21} I_1 + Z_{22} I_2$$

Now, let, $I_2 = 0$,

\therefore Circuit,

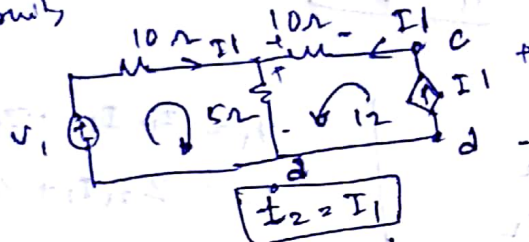

$$V_1 = 10 I_1 + 5(I_1 + I_1)$$

$$V_1 = 10 I_1 + 10 I_1$$


$$V_1 = 20 I_1$$

$$\therefore \frac{V_1}{I_1} = Z_{11} = 20$$


$$\therefore V_{cd} = 10 I_1 + 5(I_1 + I_1) = 0$$

$$V_{cd} = -20 I_1$$
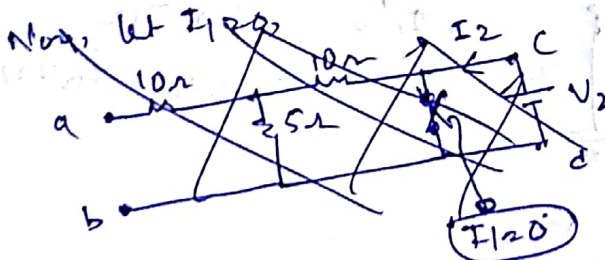
$$\therefore \frac{V_{cd}}{I_1} = -20 = Z_{21}$$



Now, let $I_1 = 0$,

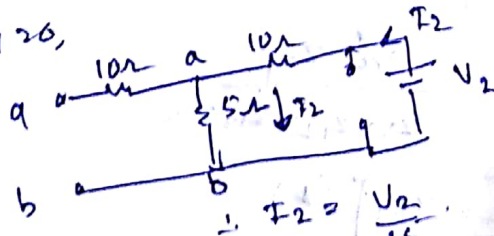

$$I_2 = \frac{V_2}{15}$$

$$\therefore \frac{V_2}{I_2} = Z_{22} = 15$$



$$V_2 = 5 \times I_2$$

$$\therefore \frac{V_2}{I_2} = Z_{12} = 5$$

$$\therefore Z = \begin{bmatrix} 20 & -5 \\ -20 & 15 \end{bmatrix}$$

(A).

(A) (5C) reciprocity

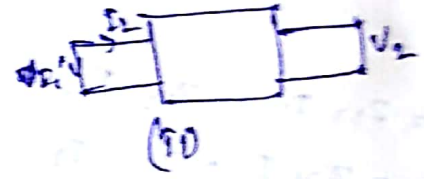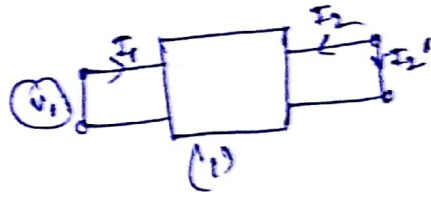

$$\begin{aligned} I_2' &= I_1' \\ V_2 &= V_2 = V_S \end{aligned}$$

for reciprocity.

(E)

$$V_1 = Z_{11} I_1 + Z_{12} I_2$$

$$V_2 = Z_{21} I_1 + Z_{22} I_2$$

$$V_1 = V_S$$

$$V_2 = 0$$

$$I_2 = -I_2'$$

$$V_S = Z_{11} I_1 - Z_{12} I_2'$$

$$0 = Z_{21} I_1 - Z_{22} I_2'$$

$$I_1 = \frac{Z_{22}}{Z_{21}} I_2'$$

$$\therefore V_S = \left(\frac{Z_{11} \times Z_{22}}{Z_{21}} - Z_{12} \right) I_2'$$

$$I_2' = \frac{V_S \times Z_{21}}{Z_{11} \times Z_{22} - Z_{12} Z_{21}}$$

$$\therefore I_2' = I_1'$$

$$\frac{V_S Z_{12}}{Z_{11} Z_{22} - Z_{12} Z_{21}} = \frac{V_S Z_{21}}{Z_{22} Z_{11} - Z_{12} Z_{21}}$$

$$\therefore \boxed{Z_{12} Z_{22} = Z_{21} Z_{11}} \quad (A)$$

$$V_1 = Z_{11} I_1 + Z_{12} I_2$$

$$V_2 = Z_{21} I_1 + Z_{22} I_2$$

$$V_1 = 0$$

$$V_2 = V_S$$

$$I_1 = -I_1'$$

$$0 = -Z_{11} I_1' + Z_{12} I_2$$

$$I_2 = \frac{Z_{11}}{Z_{12}} I_1'$$

$$V_S = Z_{21} I_1 + Z_{22} I_2$$

$$V_S = \left(\frac{Z_{22} Z_{11}}{Z_{12}} - Z_{21} \right) I_1'$$

$$I_1' = \frac{V_S \times Z_{12}}{Z_{22} Z_{11} - Z_{12} Z_{21}}$$