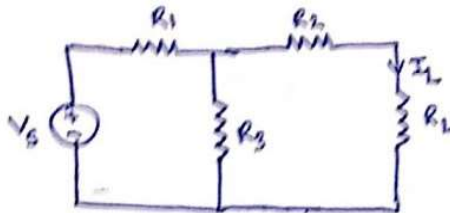


## Network Theorems


### 1. Thevenin's Theorem:

#### • Statement
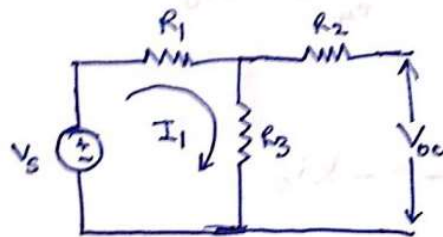
#### Explanation



Step 1: Remove  $R_L$  to find  $V_{oc}$  (open circuit voltage)




$$V_{oc} = I_1 R_3$$

$$= \frac{V_s}{R_1 + R_3} R_3$$

Step 2: To find  $R_{th}$

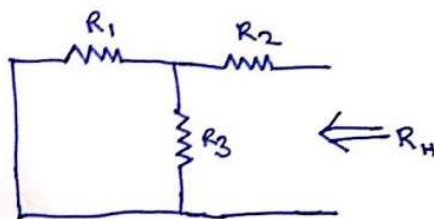
- a) if only independent source exist, deactivate each source ~~and~~ internal resistance.



$$R_{th} = R_2 + \frac{R_1 R_3}{R_1 + R_3}$$

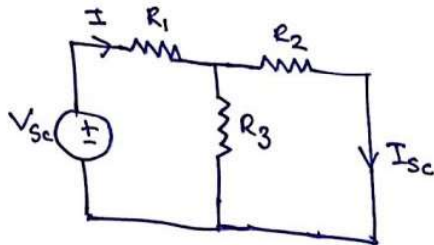- b) If both dependent and independent source exist.  
Calculate  $I_{sc}$ .

$$R_{th} = \frac{V_{oc}}{I_{sc}} \Omega$$



$$I_{sc} = I \frac{R_3}{R_2 + R_3}$$

$$I = \frac{V_s}{R_1 + \frac{R_2 R_3}{R_2 + R_3}}$$


- c) if only dependent source exist.

Connect one external voltage source of  $V_{dc}$  which flows  $I_{dc}$ . Calculate  $R_{th} = \frac{V_{dc}}{I_{dc}} \Omega$ .

Step 3:


Reconnect  $R_L$  to find  $I_L$

Thevenin's Equivalent Circuit

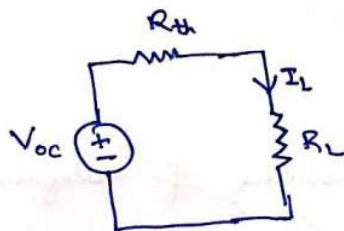

$$I_L = \frac{V_{oc}}{R_{th} + R_L}$$

## Norton's Equivalent Circuit

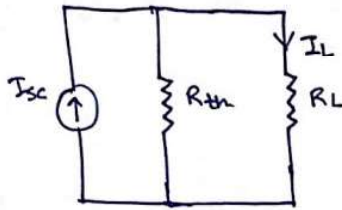

$$I_L = I \frac{R_{th}}{R_{th} + R_L}$$

## Thevenin's Theorem:

A linear active network consisting of independent and/or dependent voltage ~~src~~ and current source and linear bilateral network elements can be replaced by an equivalent circuit consisting of a voltage source in series with a resistance, the voltage source being the open circuit voltage across the open circuited node terminals and the resistance being the internal resistance of the source network, looking through the open circuited node terminals.


## Norton's Theorem:

A linear active network consisting of independent and/or dependent voltage and current source and linear bilateral network elements can be replaced by an equivalent circuit consisting of current source in parallel with a resistance, the current source being the short circuited current across the

short circuited terminal and the resistance being the internal resistance of the source network, looking through the open circuited node terminals.


### Problems:

1.

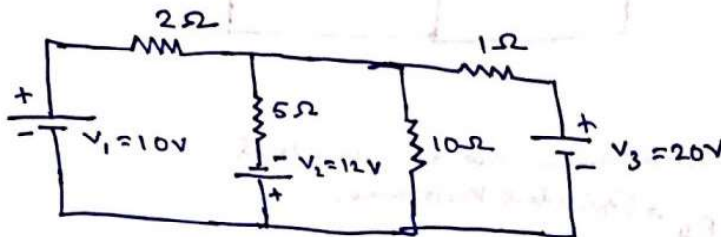

Find the current ~~the~~ through  $10\Omega$  resistor using Thevenin's Theorem.

Sol: Remove  $10\Omega$

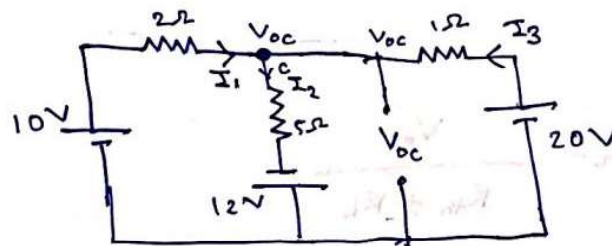

At node c,

$$I_1 + I_3 - I_2 = 0$$


$$\Rightarrow \frac{10 - V_{oc}}{2} + \frac{20 - V_{oc}}{1} - \frac{V_{oc} + 12}{5} = 0$$

$$\Rightarrow 50 - 5V_{oc} + 200 - 10V_{oc} - 2V_{oc} + 24 = 0$$

$$\Rightarrow V_{oc} = 13.29 \text{ V}$$

~~To find~~

To find  $R_{th}$

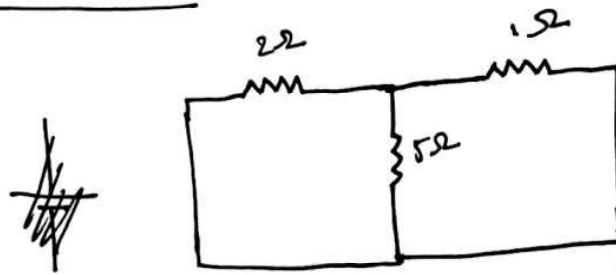

∴ the resistances are in parallel.

$$\therefore R_{th} = \frac{1}{\frac{1}{2} + 1 + \frac{1}{5}}$$

$R_{th} \rightarrow \text{Equivalent Resistance}$

$$= \frac{1}{\frac{5+10+2}{10}} = \frac{10}{17} \Omega$$

$$\therefore I_L = \frac{V_{oc}}{R_{th} + R_L}$$

$$= \frac{13.29}{\frac{10}{17} + 10} \text{ A}$$

$$= 1.26 \text{ A}$$